

3 (Sem-5) ELE M 5

2017

ELECTRONICS

(Major)

Paper : 5.5

(Network Analysis)

Full Marks : 60

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*


1. Give objective-type answer to the following : 1×7=7
- (a) What do you understand by passive element of a network?
 - (b) What is the internal impedance of an ideal voltage source?
 - (c) Define the tree of a network.
 - (d) Write down the expression for energy consumed in a capacitor.
 - (e) What is the value of Laplace transform of t^n ?
 - (f) What is decibel unit of measurement?
 - (g) Write down the expression for Fourier coefficient b_n .

8A/303

(Turn Over)

2. Give very short answers to the following (any four) : $2 \times 4 = 8$
- Derive an expression for resonance frequency of a series $R-L-C$ network.
 - Evaluate Laplace transform of an integral.
 - Define poles and zeros of a network function.
 - What is band elimination filter?
 - What is network synthesis?

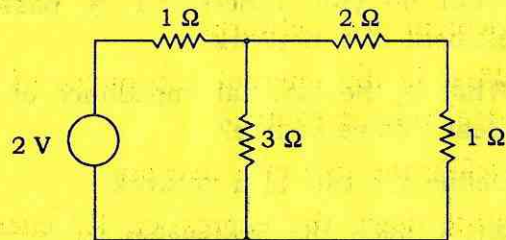3. Write short answers to any three of the following : $5 \times 3 = 15$
- For the network given below, find out Thevenin's equivalent network :



- Evaluate Laplace transform of the following :
 - $\cosh at$
 - $\frac{d}{dt} f(t)$

- State and prove the maximum power transfer theorem.
- Draw the circuit diagram of a second-order Butterworth filter and discuss briefly about the circuit.
- Discuss briefly about symmetrical and lattice networks with necessary diagram.

4. Answer any three of the following : $10 \times 3 = 30$

- Synthesize the one-port $L-C$ network using Foster's second form of equivalent network and evaluate the elements of the network.
- For a band-pass filter, show that

$$f_0 = \sqrt{f_1 f_2}$$

where f_0 is cut off frequency and f_1 and f_2 are two bands of frequency of the filter.

- Derive the short circuit admittance parameter of a two-port network.
- Write short notes on the following :
 - Passive π and T section filter
 - Fourier analysis of a periodic signal
