

Total No. of printed pages = 4

3 (Sem 3) ELE

2015

ELECTRONICS

(General)

(Linear Active Circuits and Digital Systems)

Full Marks – 40

Time – Two hours

The figures in the margin indicate full marks
for the questions.

1. Choose the correct answer from the multiple choices given for each question : $1 \times 4 = 4$
 - (a) A transistor that can be used in enhancement mode is
 - (i) npn transistor
 - (ii) UJT
 - (iii) JFET
 - (iv) MOSFET

[Turn over

(b) The output impedance of an ideal opamp is

- (i) 50 ohm (ii) 100 ohm
(iii) Infinite (iv) Zero

(c) A device that converts from decimal to binary number is called

- (i) Encoder
(ii) Decoder
(iii) Converter
(iv) None of the above

(d) How many inputs can be supplied to a logic circuit with a fan in factor of four ?

- (i) Two (ii) Three
(iii) Four (iv) Eight

2. Answer the following : 2×3=6

(a) Define offset (Input) voltage and slew rate of an opamp.

(b) Discuss the advantages of JFET.

(c) Convert the following :

- (i) 37_{16} to binary
(ii) 11_8 to binary

3. Answer the following :

(a) Give the general theory of feedback. Explain different types of negative feedback.

2+3=5

Or

What is Barkhausen criterion for oscillator ? Draw the circuit diagram of phase shift oscillator.

2+3=5

(b) Minimize the following Boolean function $f(A,B,C) = \overline{A}B + \overline{A}BC + ABC + ABC$ using Karnaugh map method. 5

Or

What do you mean by half adder and full adder ? Describe briefly the function of full adder with its logic circuit and truth table.

2+3=5

4. Answer the following :

(a) Mention some characteristics of an ideal opamp. Derive the relation for the gain of an opamp connected in non-inverting mode.

2+3=5

Or

Explain briefly, the working principle of a Unijunction Transistor (UJT). 5

- (b) What are the different types of logic gates ?
Realize the logic functions NOT and AND
using only NAND gates. 1+4=5

Or

Describe briefly the different types of
semiconductor memories. 5

5. Write short notes on any two : 5×2=10

- (a) Active filter
- (b) Distortion in amplifier
- (c) Multiplexer and demultiplexer
- (d) Flip-Flop.