

Total No. of printed pages = 4

3 (Sem 1) ELE M2

2015

ELECTRONICS

(Major)

Paper : 1.2

(Solid State Devices)

Full Marks – 60

Time – Three hours

The figures in the margin indicate full marks for the questions.

1. Answer all questions : $1 \times 7 = 7$
- (a) What are the different types of extrinsic semiconductors ?
 - (b) Which group of elements are considered to be suitable for use as semiconductors ?
 - (c) What is the barrier potential in terms of voltage in case of silicon diode ?
 - (d) How is base current related to emitter current in case of a BJT ?

[Turn over

- (e) Which mode of operation of the BJT is suitable for use as power amplifier?
- (f) In case of a diode, at constant temperature of forward voltage increases what will happen to the reverse saturation current?
- (g) If negative feedback is used, what will happen to distortion?

2. Answer the following questions : $2 \times 4 = 8$

- (a) What are the two different types of breakdowns observed in case of diode?
- (b) Write the diode current equation and identify the different components / variables / constants etc. used in the expression.
- (c) What is PIV?
- (d) What is slew rate in case of an Op-AMP?


3. Answer any *three* questions : $5 \times 3 = 15$

- (a) Draw the V.I characteristics of the diode and identify the different sections. Write briefly about each of the sections and their significance.
- (b) Draw an arrangement showing the use of a Zener diode as a voltage regulator. Explain how voltage regulation is achieved.

28A/3 (Sem 1) ELE M2 (2)

- (c) Mention the differences between load and line regulation. Draw relevant figures and use necessary formulae.

(d) A BJT based circuit is as below :

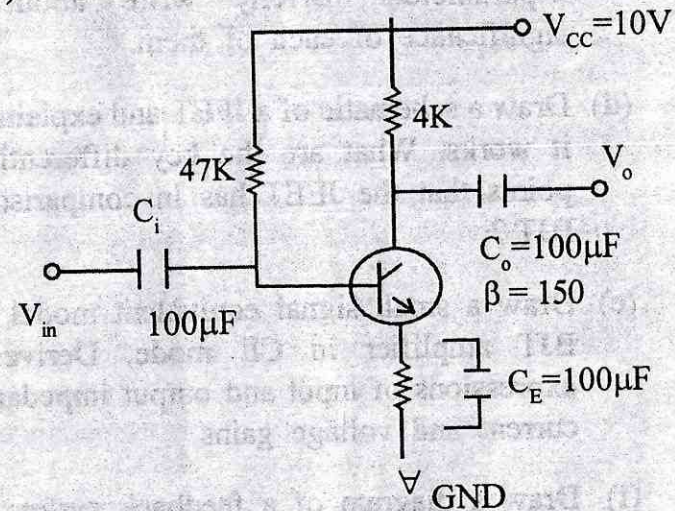

Find the voltage gain of the circuit.

- (e) Draw the circuit of an active low pass second order filter. Explain its working. What are the benefits of using active filters.

4. Answer any *three* questions : $10 \times 3 = 30$

- (a) Derive an expression for the junction capacitances of a diode showing dependence of carrier concentration and barrier width.

28A/3 (Sem 1) ELE M2 (3)

[Turn over

- (b) What is a clipper ? What are the different types ? Draw the circuits and outputs of each of them.
- (c) For a CE model BJT, determine the different h-parameters. Briefly write about the significance of each of them.
- (d) Draw a schematic of a JFET and explain how it works. What are the key differentiating points that the JEET has in comparison to BJT ?
- (e) Draw a small signal equivalent model of a BJT amplifier in CE mode. Derive the expressions of input and output impedances, current and voltage gains.
- (f) Draw a diagram of a feedback system and derive an expression for gain of the system. Using the expression, explain the advantages obtained due to the use of negative feedback.
- (g) Write short notes on (any *two*): $2 \times 5 = 10$
- (i) Schmitt trigger
 - (ii) Precision rectifier
 - (iii) Oscillator.