

Total No. of printed pages = 3

3 (Sem 3) ELE M1

2015

ELECTRONICS

(Major)

Paper : 3.1

(Linear Active Circuits)

Full Marks – 60

Time – Three hours

The figures in the margin indicate full marks
for the questions.

1. Answer the following : 1×7=7
- (a) Write the full form of JFET.
 - (b) What is CMRR of an OPAMP ?
 - (c) Define h_{12} -parameter.
 - (d) What are the disadvantages of class A amplifier ?
 - (e) Write the expression for cut off frequency of a 1st order Butterworth filter.

[Turn over

- (f) How will you define a distributed element ?
- (g) What is the value of threshold voltage of a silicon diode ?
2. Write very short answer to the following : (any four) $2 \times 4 = 8$
- (a) Discuss briefly about the parasitic capacitances in an RC-coupled amplifier.
- (b) Discuss briefly about the push pull amplifier.
- (c) Derive the expression of voltage gain of an OPAMP in its non-inverting modes of operation.
- (d) Draw the circuit diagram of an amplifier using transistor in the C-B configurations.
- (e) What is loadline ?
- (f) What is band elimination ?
3. Write short answer to any *three* of the following : $5 \times 3 = 15$
- (i) Draw the circuit diagram of a Schmitt Trigger using OPAMP and explain its working principle.
- (ii) Discuss briefly about class AB power amplifier.

- (iii) Draw the circuit diagram of an OPAMP subtractor and discuss briefly about its working principle.
- (iv) Explain about the two port representation of BJT with h-parameter.
- (v) Design a monostable multivibrator using IC 555 timer and explain its working principle.
4. Answer the following : $10 \times 3 = 30$
- (a) Explain the working principle of a JFET with necessary diagram and explain its working principle.
- (b) Draw the circuit diagram of an amplifier in C-E configuration using voltage divider bias condition and explain the working principle of the circuit.
- (c) Design a Wein Bridge Oscillator and discuss briefly about its working principle.
- (d) Write short notes on :
- (i) Band pass active filter
- (ii) Phase-shift oscillator.