

3 (Sem-1) CSC M 2

2016

COMPUTER SCIENCE

(Major)

Paper : 1.2

(Basic Electronics)

Full Marks : 60

Time : 3 hours

*The figures in the margin indicate full marks
for the questions*

1. Choose the correct option : 1×7=7

(a) With the increase in temperature the resistivity or specific resistance of semiconductors

(i) increases

(ii) decreases

(iii) remains unchanged

(b) Which of the following is a unipolar device?

(i) *p-n-p* transistor

(ii) IC

(iii) MOSFET

A7/51

(Turn Over)

(2)

- (c) At fixed temperature, Ohm's law is obeyed in case of
- (i) conductors
 - (ii) electrolytes
 - (iii) semiconductors
- (d) Which of the following is not a universal gate?
- (i) AND
 - (ii) NOR
 - (iii) NAND
- (e) The L-section filter with inductance L and capacitor C is connected at the output of a rectifier in which of the following ways?
- (i) C in series, L in parallel connection
 - (ii) L in series, C in parallel connection
 - (iii) Both L and C are in series connection
- (f) The capacitance of a parallel-plate capacitor can be increased by
- (i) reducing its plate area
 - (ii) filling the entire space between the plates with a dielectric material of dielectric constant $k > 1$
 - (iii) increasing spacing between the plates

(3)

- (g) Boolean algebra was first developed by
- (i) Bertrand Russell
 - (ii) George Boole
 - (iii) Claude Shannon

2. Answer the following questions : 2×4=8

- (a) How is an $n-p-n$ transistor biased in CB configuration in order to operate it in active region?
- (b) State the function of a filter circuit in rectifier.
- (c) Differentiate between combinational and sequential circuits.
- (d) Why are multiplexers called data selectors?

3. Answer any *three* of the following questions : 5×3=15

- (a) How are p -type and n -type semi-conductors made? Distinguish between ordinary resistor and LDR.
- (b) Simplify the following Boolean expression using K-map :

$$F(A, B, C, D) = \Sigma (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$

(4)

- (c) Draw the circuit diagram of transistor in CB and CE configurations using either *p-n-p* or *n-p-n* transistor with proper d.c. biasing. With same input signal, which of them will give higher voltage gain? Justify your answer.
- (d) Draw the logic diagram of a binary half adder. Write the truth table and develop the expression for sum and carry.

4. Answer any *three* of the following questions :

10×3=30

- (a) What are the basic rules to convert SOP expression to POS form and POS expression into SOP form? Find the POS and SOP forms of the following expression :

$$X = \sum m(0, 1, 3, 6, 8, 13, 15)$$

Which one is more cost effective?

- (b) What are digital demultiplexers? Explain their principle of operation and applications in communication system.

(5)

- (c) State the rules for changing positive logic to its corresponding negative logic. Show diagrammatically with proper symbol, how you will realize the following :
- (i) AND function using NAND gates only
 - (ii) OR function using NOR gates only
 - (iii) NOT function using NAND gates or NOR gates
 - (iv) AND function using NOR gates
- (d) State the different types of shift registers. Considering two 4-bit shift registers, explain with a block diagram how the data transfer is made between them.
- (e) Write short notes on any *two* of the following :
- (i) LED
 - (ii) Operational amplifier
 - (iii) Decoder
 - (iv) S-R flip-flop
